

# thanks to plug-in coils...

# ONE RECEIVER ALL BANDS

By **PHILIP E. HATFIELD**, W9GFS

Receiving Tube Dept., General Electric Co., Owensboro, Ky.


**M**OST of today's short-wave receivers are truly sensitive and reliable devices, but they are also rather complex and expensive for the beginner to construct. Here's a simple receiver, using one compactron tube, that will give you long-wave, broadcast-band, and short-wave reception. If you are considering putting your first receiver together, this one is for you. If you have an amateur-band-only receiver, this unit will fill in some of the "holes" in the spectrum. Finally, if you already have a general-coverage receiver, this set will make a good "auxiliary" to tuck away on a corner of the desk just in case your "big" one quits.

Use of a compactron allows a lot of receiver to be contained in a small box without undue crowding. The frequency range covered is from 250 kc. all the way to 16 mc.; and, since plug-in coils are used, it's possible to extend the range in either direction. Plenty of headphone volume is provided, and many signals will operate the built-in speaker in a very satisfactory manner.


**The Circuit.** The 6AF11 compactron contains two triodes and a pentode. One triode is used as a regenerative detector, the other as an audio voltage amplifier, and the pentode as an audio power amplifier.

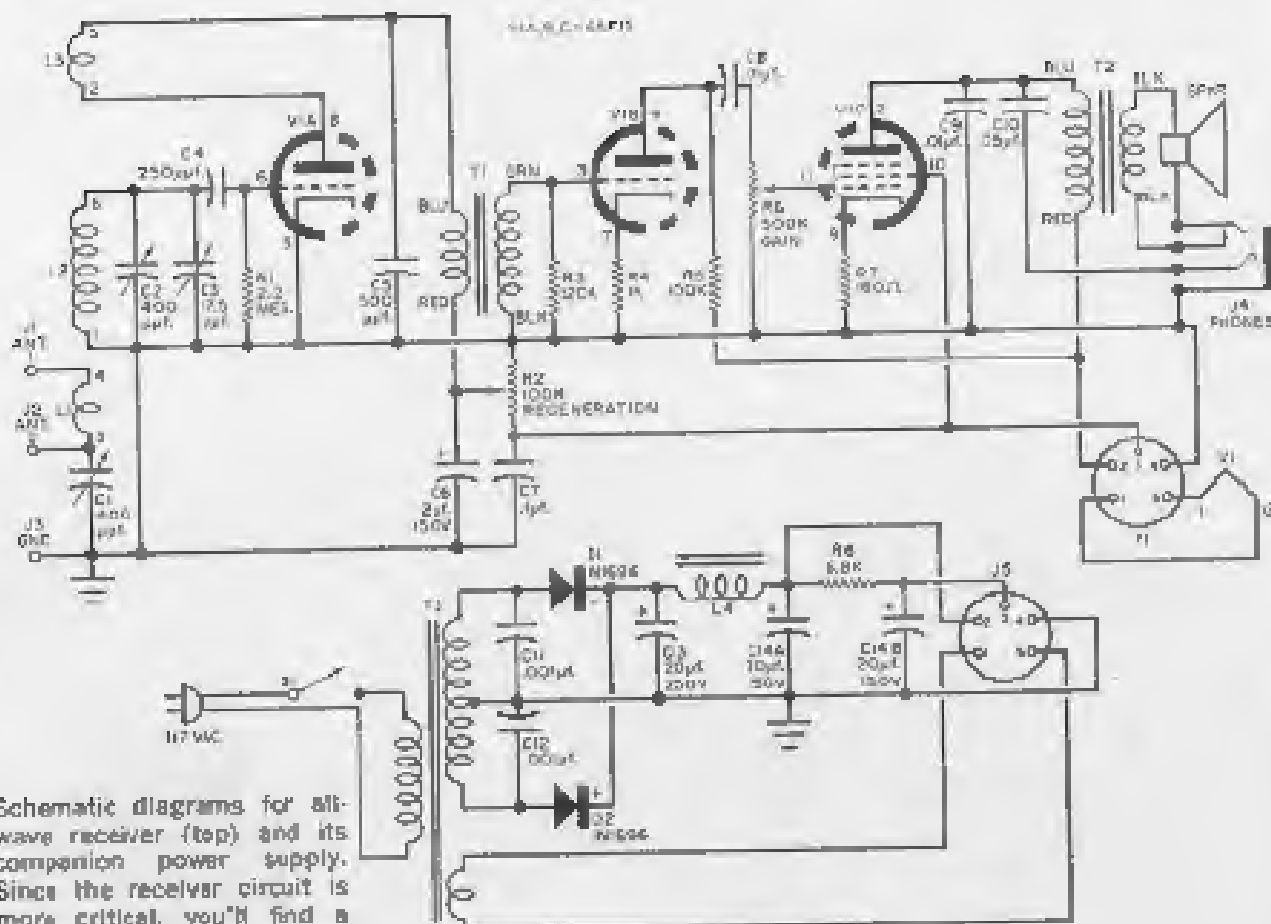Plug-in coils containing primary (*L1*), secondary (*L2*), and tickler (*L3*) windings determine the frequency range. Tuning is done with a relatively large variable capacitor (*C2*) to allow covering a wide range of fre-





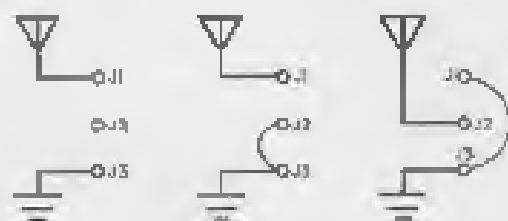Schematic diagrams for all-wave receiver (top) and its companion power supply. Since the receiver circuit is more critical, you'll find a pictorial diagram of it on page 81; you should be able to wire up the power supply without difficulty by following parts layout shown in photos on pages 82 and 83.



Versatility is the word on antenna hookups for this receiver, and three possible configurations appear at left.

## PARTS LIST

C1, C2—400- $\mu$ f. variable capacitor (Allied 41 E109 or equivalent)  
 C3—17.5- $\mu$ f. variable capacitor (Hammarlund RF-35 or equivalent)  
 C4—250- $\mu$ f. mica capacitor  
 C5—500- $\mu$ f. mica capacitor  
 C6—2- $\mu$ f., 150-v.d.c. electrolytic capacitor  
 C7—0.1- $\mu$ f., 400-volt paper capacitor  
 C8, C9—0.01- $\mu$ f., 1000-volt ceramic capacitor  
 C10—0.05- $\mu$ f., 400-volt paper capacitor  
 C11, C12—4,001- $\mu$ f., 1000-volt ceramic capacitor  
 C13—20- $\mu$ f., 250-v.d.c. electrolytic capacitor  
 C14a/C14b—Dual 20/20- $\mu$ f., 150-v.d.c. electrolytic capacitor  
 D1, D2—1N1696 diode  
 J1, J2, J3—Insulated binding post  
 J4—"Closed and transfer" phone jack (Mallory 703B or equivalent)  
 J5—5-prong socket  
 L1, L2, L3—Plug-in coil—see page R2 for details  
 L4—20-henry, 15-ma. choke (Chicago Stancor C-1515 or equivalent)  
 P1—5-prong plug  
 R1—2.2-megohm,  $\frac{1}{2}$ -watt resistor  
 R2—100,000-ohm potentiometer, linear taper  
 R3—120,000-ohm,  $\frac{1}{2}$ -watt resistor  
 R4—1000-ohm,  $\frac{1}{2}$ -watt resistor

R5—100,000-ohm,  $\frac{1}{4}$ -watt resistor  
 R6—500,000-ohm potentiometer, audio taper  
 R7—100-ohm,  $\frac{1}{2}$ -watt resistor  
 R8—6800-ohm,  $\frac{1}{2}$ -watt resistor  
 S1—S.p.s.t. toggle switch  
 SPKR—2 $\frac{1}{2}$ " PM speaker, 3.2-ohm voice coil  
 T1—Interstage transformer, 1:3 turns ratio (Chicago Stancor A-53 or equivalent)  
 T2—Output transformer; primary, 10,000 ohms; secondary, 4 ohms (Stancor A3879 or equivalent)  
 T3—Power transformer; primary, 117 volts a.c.; secondaries, 250 volts CT @ 25 ma. and 6.3 volts @ 1.0 amp (Stancor PS-8416 or equivalent)  
 V1—6AF11 tube  
 4—Six-prong coil forms,  $\frac{1}{4}$ " in diameter, 2 $\frac{1}{2}$ " long (Allied 71 H 724 or equivalent)  
 1—6" x 3" x 4" chassis box (LMB T-F781 or equivalent)  
 1—6" x 2 $\frac{3}{4}$ " x 2 $\frac{1}{4}$ " chassis box, gray hammer-tone finish (Bud CU-2104-A or equivalent)  
 4—4-pin sockets  
 Misc.—Dial, knobs, aluminum for chassis, wire for coils, hookup wire, sockets for V1, line cord and plug, 5-conductor power cable with 5-pin socket and plug, hardware, solder, etc.


For best results, you'll want to follow this pictorial diagram when you construct the all-wave receiver. Wiring should progress smoothly once the chassis plate is cut and drilled and the major parts have been mounted.

ed receiver (below).  
chassis plate in place.  
or for coils is in other  
of the chassis box.

The antenna coupling circuit is purposely designed for versatility. Straight inductive coupling, series tuning, or parallel tuning are possible, depending on the connections to jacks J1, J2, and J3 (see antenna hookup diagram at left). This can be quite helpful in increasing

For maximum audio output, the headphones are operated from the pentode section of the compactron, and the phone jack (54) is arranged to disconnect the speaker when the phones are in use.

1964 Edition

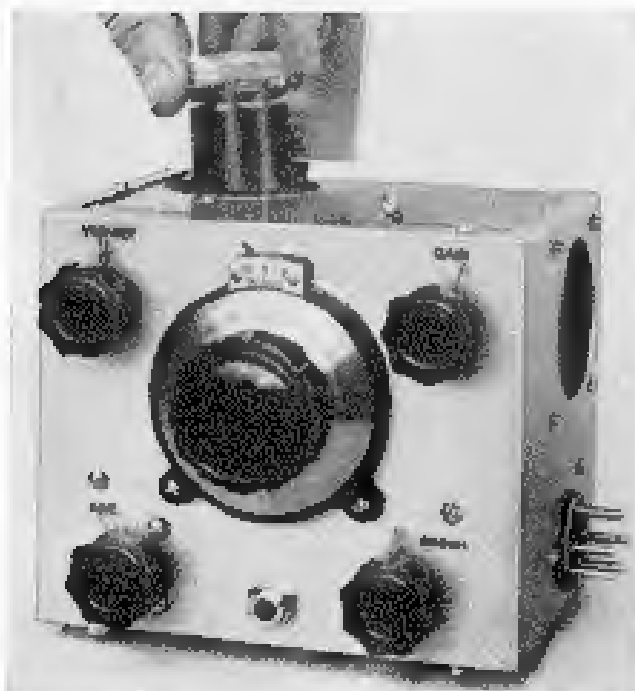

No likelihood of losing coils with this set—one, inserted through a trap door (far left), is always in use; the other three (above) rest in empty sockets mounted on aluminum flange at rear of cabinet.

before the cabinet is "buttoned up."

To reduce sheet metal bending to a minimum, the chassis proper is a flat plate, cut to make a fairly snug fit, and then fastened in place with four small angle brackets. All mounting holes should be cut in this plate and the chassis box before the plate is bolted in place.

After the holes have been drilled, all of the parts should be mounted, since they are all readily accessible for wiring in any sequence. In mounting the 400- $\mu$ f. antenna tuning capacitor (C1), flat washers should be used between the panel and the capacitor frame to insure that the screws don't extend through the

Winding data for receiver's four plug-in coils appears below. All of them are close-wound, except for the long-wave coil (250-600 kc.) at far right; full information on how to wind this particular coil appears in text. Vary spacing (d2) on the first three coils by sliding L3 back and forth on the form until regeneration seems "smoothest," then apply cement to hold coils in place.

	4.8-16.0 mc.	1.75-6.1 mc.	510-1750 kc.	250-600 kc.
L1	5 turns #26 enameled	8 turns #26 enameled	18 turns #30 enameled	30 turns #28 DCC
d1	$\frac{1}{4}$ "	$\frac{1}{16}$ "	$\frac{1}{4}$ "	
L2	8 turns #22 enameled	23 turns #21 enameled	100 turns #30 enameled	200 turns #28 DCC
d2	$\frac{1}{4}$ "	$\frac{1}{16}$ "	$\frac{1}{16}$ "	
L3	3 turns #26 enameled	4 turns #26 enameled	8 turns #30 enameled	10 turns #28 DCC

